

Counters

15/10/13


Revanth Gopi Konakanchi
Dept of CSE | 120101036

Anil Kumar Ravuru
Dept of CSE | 120101059

Prudhvi Raj Chowhan
Dept of CSE | 11010131

Clear Register is used to clear the previous existing values when necessary to do so. These are of two types

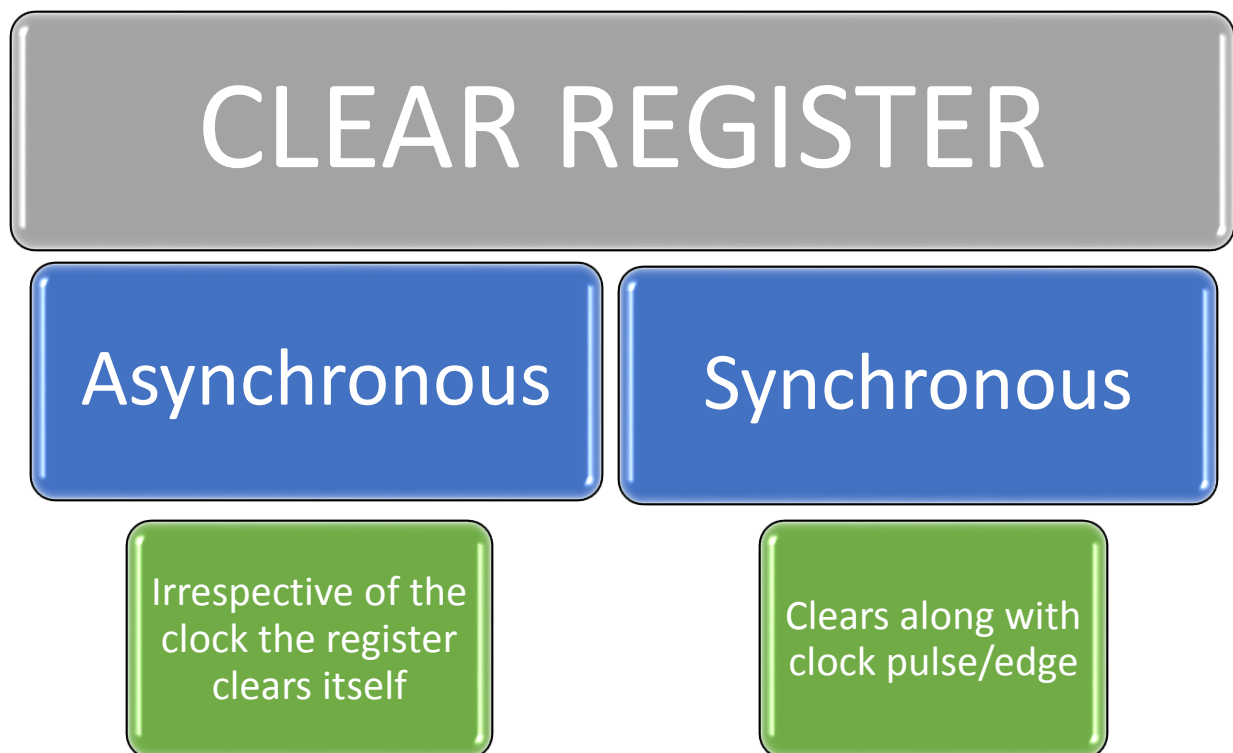1. Asynchronous Register
2. Synchronous Register



COUNTERS:

Counters are classified into 3 types

1. Shift Register
2. Ripple Counter
3. Synchronous Counter


SHIFT REGISTER

shift register is a cascade of flip flops, sharing the same clock, in which the output of each flip-flop is connected to the data input of the next flip-flop in the chain, resulting in a circuit that shifts by one position the bit array stored in it.

Example



➤ Block Diagram for shift register

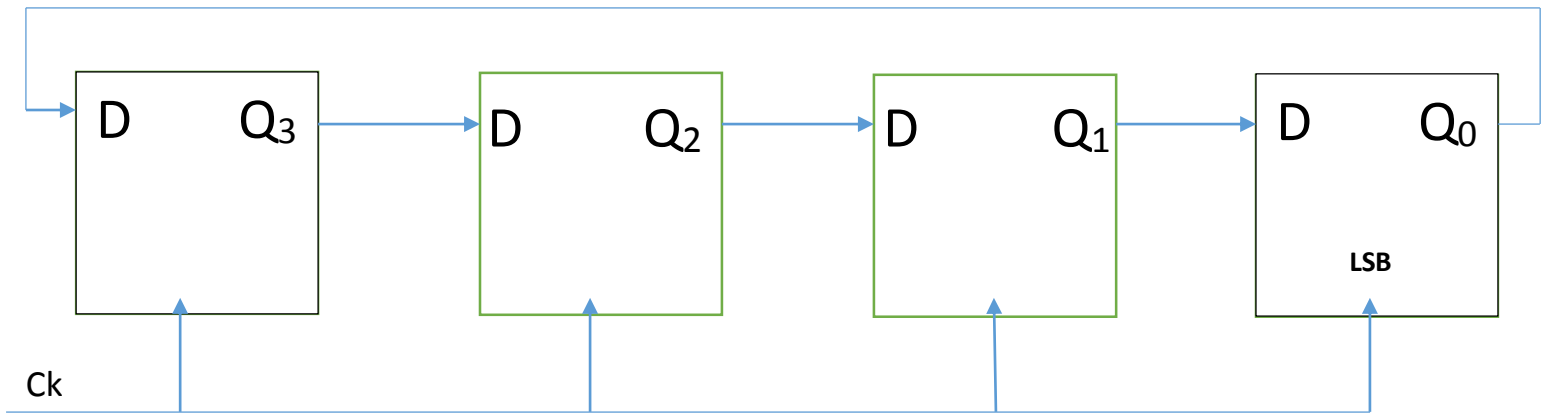

Consider the above example

Initially $Q_3Q_2Q_1Q_0 = 1001$


After one cycle $Q_3Q_2Q_1Q_0 = 1100$ (Q_i shifts to Q_{i-1})

After second cycle $Q_3Q_2Q_1Q_0 = 0110$

After third cycle $Q_3Q_2Q_1Q_0 = 0011$


- In normal shift register maximum 4 different outputs are possible.

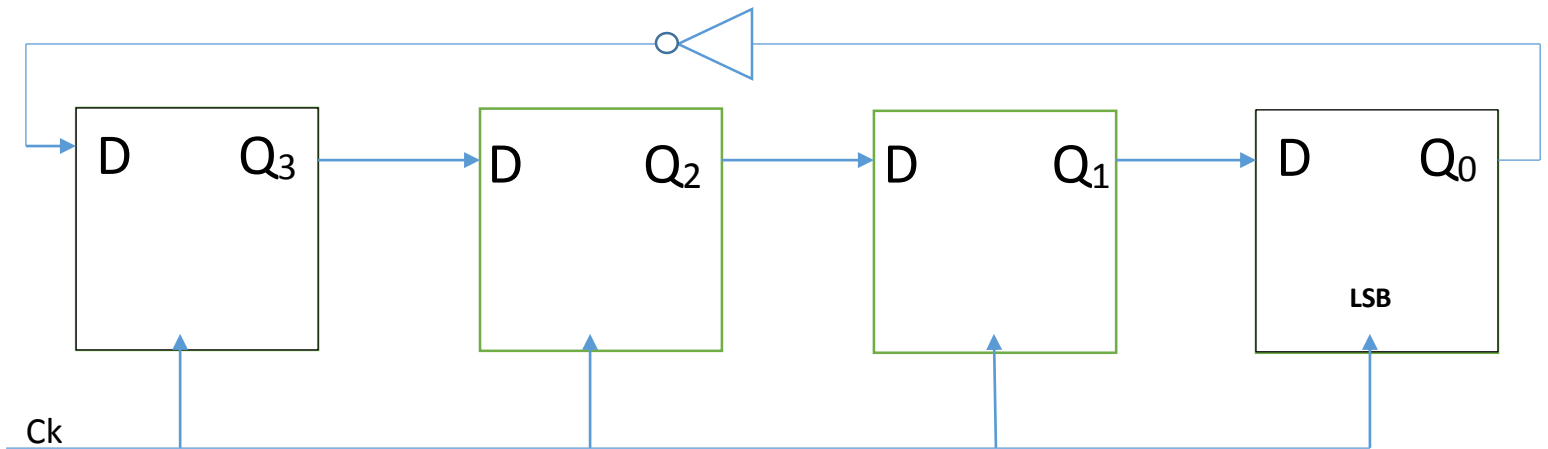Johnson Counter (special case of shift register)



In the above example

Initially $Q_3Q_2Q_1Q_0 = 1001$

 

In this counter
maximum 8
different outputs
are possible.

RIPPLE COUNTERS

A ripple counter is a counter in which state transitions of one or more flip flops are triggered by the outputs of other flip flops in the circuit.

- Ripple counter is Asynchronous counter


4 BIT BINARY UP COUNTER

Q_3	Q_2	Q_1	Q_0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
.	.	.	.
.	.	.	.
1	1	1	1

- Q_0 always toggles
- Q_1 toggles when Q_0 changes from 1 → 0
- Q_2 toggles when Q_1 changes from 1 → 0
- Q_3 toggles when Q_2 changes from 1 → 0

4 bit binary up counter using J-K flip flop

❖ Using negative edge triggered clock

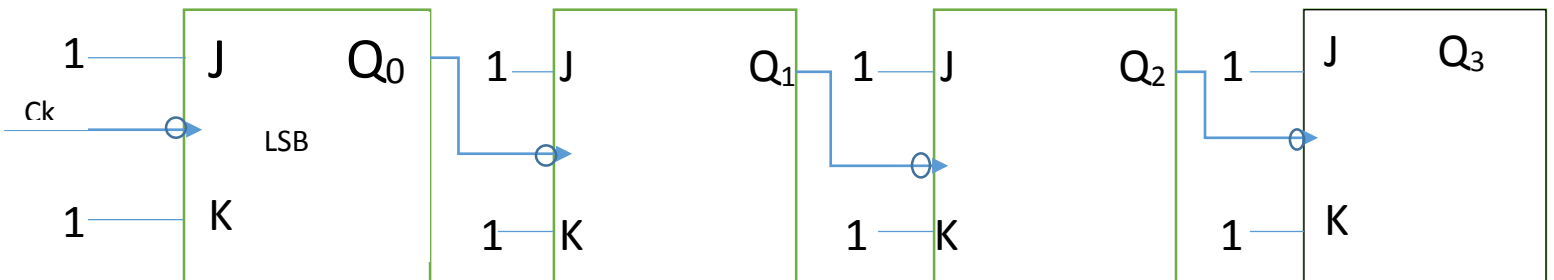


We know that when $J=K=1$ in J-K Flip-flop Output toggles

So for output Q_0 when clock is in negative edge triggered state the value toggles


Similarly for Q_1 , Q_0 acts as clock signal

Similarly for Q_2 , Q_1 acts as clock signal

 Similarly for Q_3 , Q_2 acts as clock signal



❖ Using positive edge triggered clock

 

We know that when $J=K=1$ in J-K Flip-flop Output toggles

So for output Q_0 when clock is in positive edge triggered state the value toggles

Similarly for Q_1 , Q_0 acts as clock signal

Similarly for Q_2 , Q_1 acts as clock signal

Similarly for Q_3 , Q_2 acts as clock signal


4 BIT BINARY DOWN COUNTER

Q_3	Q_2	Q_1	Q_0
1	1	1	1
1	1	1	0
1	1	0	1
1	1	0	0
1	0	1	1
1	0	1	0
.	.	.	.
.	.	.	.
0	0	0	0

- Q_0 always toggles
- Q_1 toggles when Q_0 changes from 0 → 1
- Q_2 toggles when Q_1 changes from 0 → 1
- Q_3 toggles when Q_2 changes from 0 → 1

4 Bit Binary down Counter using J-K flip-flop

❖ Using negative edge triggered clock

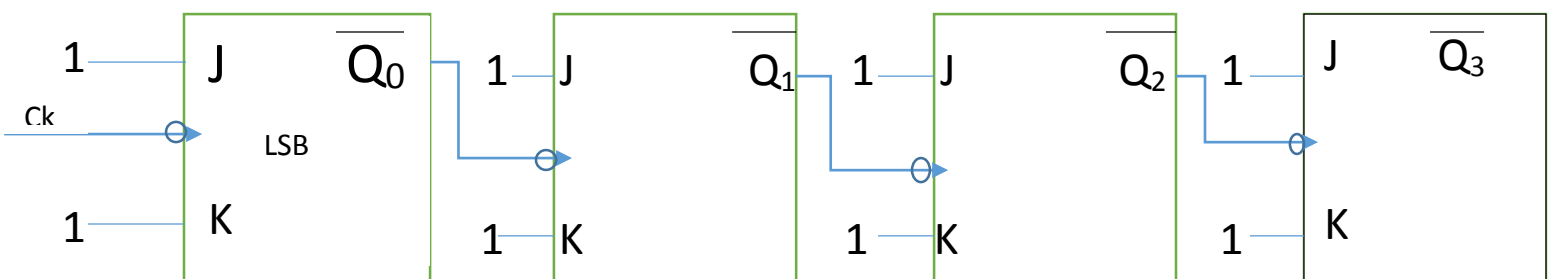

We know that when $J=K=1$ in J-K Flip-flop Output toggles


So for output Q_0 when clock is in negative edge triggered state the value toggles

Similarly for Q_1 , Q_0 acts as clock signal

Similarly for Q_2 , Q_1 acts as clock signal

Similarly for Q_3 , Q_2 acts as clock signal

❖ Using positive edge triggered clock

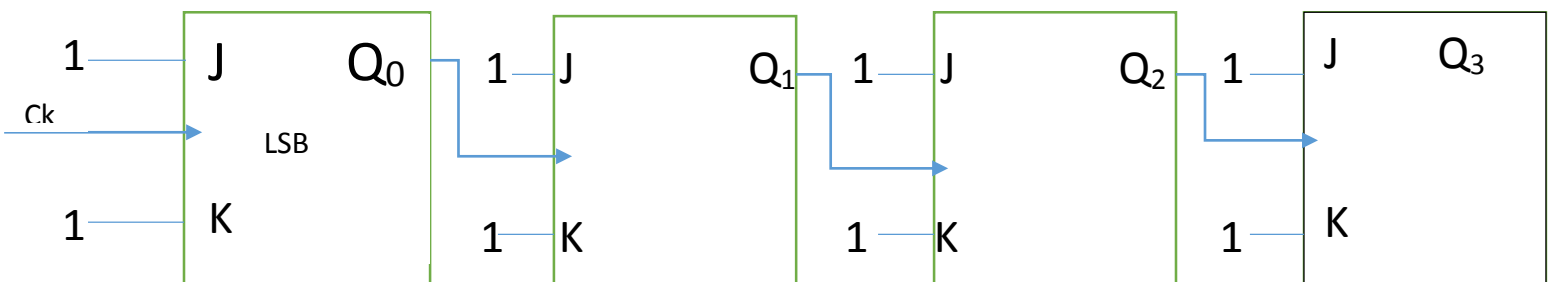

We know that when $J=K=1$ in J-K Flip-flop Output toggles


So for output Q_0 when clock is in positive edge triggered state the value toggles

Similarly for Q_1 , Q_0 acts as clock signal

Similarly for Q_2 , Q_1 acts as clock signal

Similarly for Q_3 , Q_2 acts as clock signal

Decade up counter

 


After 1001 $Q_3Q_2Q_1Q_0$ goes to 0000 instead of 1010.

So we reset the flip-flop using 1010 value

$$\text{Reset} = \overline{Q_3}\overline{Q_2}Q_1\overline{Q_0}$$

Decode down counter

 

After 0000 $Q_3Q_2Q_1Q_0$ goes to 1001 instead of 1111.

So we reset the flip-flop using 1111 value

Reset = $Q_3 Q_2 Q_1 Q_0$

Synchronous counter

Every flip-flop receives the exact same clock pulse at the exact same time (Global Clock)

3 Bit Binary up Counter

Q_2	Q_1	Q_0
-------	-------	-------

0	0	0
---	---	---

0	0	1
---	---	---

➤ Q_1 toggles in next cycle when $Q_0 = 1$

0	1	0
---	---	---

0	1	1
---	---	---

➤ Q_2 toggles in next cycle when $Q_0=Q_1=1$

1	0	0
---	---	---

1	0	1
---	---	---

1	1	0
---	---	---

1	1	1
---	---	---

0	0	0
---	---	---

