 


# Lecture Notes

Dated-08/10/13

## Master-Slave Latch(Revision)



- When clock =1 then clock in slave =0

1.Master Latch behaves as normal RS latch.

R	S	$Q_{M+1}$
0	0	$Q_M$
0	1	1
1	0	0
1	1	illegal

2. Slave latch is in hold condition as RS=00(hold)

3. As long as clock=1,the changes in input values of R and S will affect only  $Q_M$  and  $Q_S$  remains unchanged.

- When clock=0,

1. Master is on hold condition as RS=00.

2. Clock input =1 for slave latch.

**3. In slave latch,**


$$R=Q_M^C$$

$$S=Q_M$$

 **4.If  $Q_M=0$ , then  $R_S=1$  and  $S_S=0 \Rightarrow Q_S=0$  (Reset Condition) and vice-versa.**

- **Output of Master-Slave latch can only be changed when clock=1.**
- **Whatever was the last input before clock becomes 0 is captured by Master-Slave latch and output of Master Latch will be passed to Slave Latch.**
- **This combination is called Negative Edge Triggered Master-Slave Latch Combination.**
- **For the outside world, only the output of the Slave latch is available.**
- **$Q_{S+1}=S_M+R_M^C Q_S$**
- **Output of Master – Slave latch is available when clock completes its cycle.**

One's catching problem  
in NOR M-S latch.



## ONE'S CATCHING PROBLEM

- One's catching problem arise in MASTER SLAVE LATCH made up of NOR gates, i.e NOR M-S LATCH.

- RS latch made up of two NOR gates holds previous state when the inputs are 0 as it has HOLD STATE at  $R=S=0$ .
- If now set transitions to 1 then we get the state  $S=1$  and  $R=0$  which is the set condition.
- If set subsequently transitions back to 0, then again the HOLD STATE will be reached and it will now hold the value which was set previously.
- Now in the above fig at time  $T_g$  the set glitches and jumps to 1 and then back to 0 quickly,
- When the set glitches to 1 the state  $S=1$  and  $R=0$  is reached which is the SET condition so  $Q_m$  gets set to 1.
- Now subsequently when  $S$  gets back to 0 the state  $S=0$  and  $R=0$  is reached which is the HOLD CONDITION, the state with  $Q_m=1$  will be held instead of the state with  $Q_m=0$
- I.E The latch catches the 1 even though the transition is very quick.
- To avoid one's catching problem the easiest solution is to set  $S \neq R$ . As the condition  $S=R=0$  will vanish, hence no hold condition occurs at the RS latch and hence there will be no catching problem.

## **ZERO'S CATCHING PROBLEM**


- Zero's catching problem arise in NAND M-S-LATCH.
- Latch made up of NAND gets hold previous state when the inputs are 1. As it's HOLD STATE occur at  $\underline{S}=1$ ,  $\underline{R}=1$

- Its SET CONDITION is  $\underline{S}=0, \underline{R}=1$ .
- If there's a glitch that makes the transition from  $\underline{S}=1$  to  $\underline{S}=0$ , then the latch may catch the 0 and set the value of Q.
- To avoid zero's catching problem the easiest solution is to set  $S \neq R$ . As the condition  $S=R=1$  will vanish, hence no hold condition occurs at the latch and hence there will be no catching problem.

This can be achieved using D flip flop.

## D Flip Flop

Fig:-

 


D-Flip flop using NAND gates

### Characteristics:-

- Shifts one bit of data from input to output.
- Only One input required
- $Q_{N+1} = D_N$

## Master Slave Latch using D Flip Flop

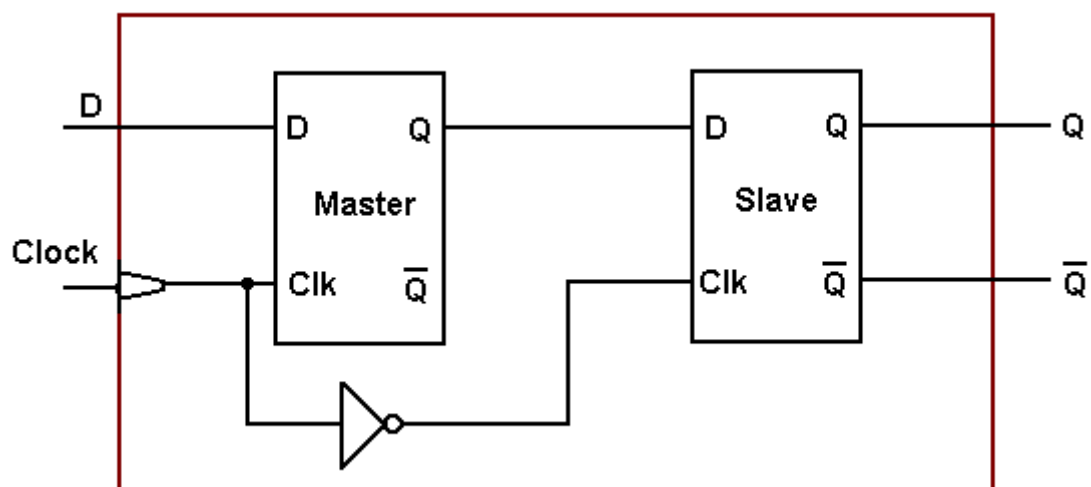


### When Clock=1 ,i.e Master Active-

1.  $R_M = D^c$  and  $S_M = D$
2.  $Q_{S+1} = D$

**Proof:**

$$\begin{aligned} Q_{S+1} &= S_M + R_M^c Q_S \\ &= D + D Q_S \text{ (Since } (D^c)^c = D \text{)} \\ &= D(1 + Q_S) \\ &= D \end{aligned}$$
 
## Master Slave Latch using J –K Flip Flop



- It is same as the R-S flip –Flop except we can also give J=1 and K=1 as input.
- When J=1 and K=1,  $R_M = Q_S$

$$S_M = Q_S^c$$

$$Q_{S+1} = Q_S^c$$

$$\text{Proof : } Q_{S+1} = S_M + R_M^c Q_S$$

$$= Q_S^c + Q_S^c Q_S$$

$$= Q_S^c (1 + Q_S)$$

$$= Q_S^c$$

Hence output will toggle.

- In General,  $S_M = JQ_S^C$  and  $R_M = KQ_S$

- $Q_{S+1} = JQ_S^C + K^C Q_S$

**Proof:**  $Q_{S+1} = S_M + R_M^C Q_S$


$$= JQ_S^C + (KQ_S)^C Q_S$$

$$= JQ_S^C + (K^C + Q_S^C)Q_S$$

$$= JQ_S^C + K^C Q_S + Q_S^C Q_S$$

$$= JQ_S^C + K^C Q_S$$
 
## Timing Diagram For JK Master Slave Flip Flop



By:

Akshay Verma-120101007

Khan Akib Naweel -120101034

Manish Sharma-120101040